

## I B.Tech- I Semester Supply Examinations, NOV -2022

## Basic Electrical Engineering-I

(Com. to ECE Branch Only)

Time :3 Hours

Max.Marks:70


Answer any five Questions one Question from Each Unit  
All Questions Carry Equal Marks

## UNIT -I

- 1 A) Classify the electrical circuit parameters. 6M  
B) Explain the Electric charge and current. 4M  
C) Explain the electric energy and potential. 4M

OR

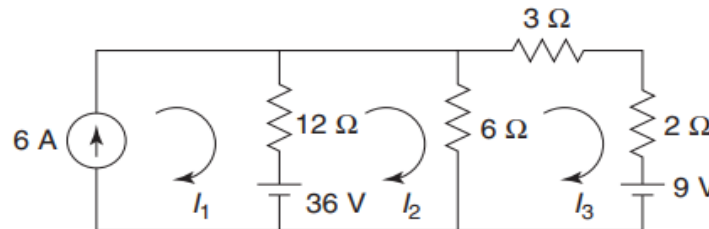- 2 A) Derive the expressions for resistances when a network is converted from delta to star and star to delta transformation. 7M  
B) Find the current through the  $2\ \Omega$  resistor in the network of fig. using mesh analysis.



## UNIT -II

- 3 A) Illustrate the terms associated with periodic functions for a sinusoidal waveform: Time period, Angular velocity and frequency, RMS value, Average value, Form factor and peak factor 7M  
B) Derive the mathematical expressions for a sinusoidal quantity response to a series connected elements resistance and inductance (R-L) across a sinusoidal excitation. 7M

OR

- 4 A) A 60 Hz sinusoidal voltage  $v = 141 \sin \omega t$  is applied to a series R-L circuit. The values of the resistance and the inductance are  $3\ \Omega$  and  $0.0106\ \text{H}$  respectively. (i) Compute the r.m.s. value of the current in the circuit and its phase angle with respect to the voltage. (ii) Write the expression for the instantaneous current in the circuit. (iii) Compute the r.m.s. value and the phase of the voltages appearing across the resistance and the inductance. (iv) Find the average power dissipated by the circuit. (v) Calculate the p.f. of the circuit. 7M  
B) Develop the mathematical expressions for a sinusoidal quantity response to an element of a pure resistance connected across a sinusoidal excitation. 7M


## UNIT -III

- 5 A) Derive the mathematical expression for coefficient of coupling (K) in a magnetic circuit. 7M

- B) Two coils, A and B, have self-inductances of  $120 \mu\text{H}$  and  $300 \mu\text{H}$  respectively. A current of  $1 \text{ A}$  through coil A produces flux linkages of  $100 \mu\text{Wb}$  turns in coil B. Determine (i) the mutual inductance between the coils (ii) the coupling coefficient and (iii) the average e.m.f. induced in coil B if a current of  $1 \text{ A}$  in coil A is reversed at a uniform rate in  $0.1 \text{ sec}$  7M

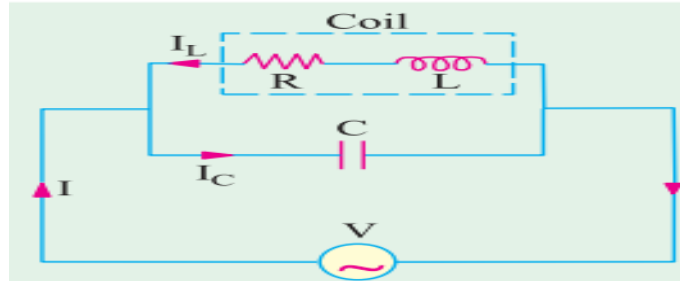**OR**


- 6 A) Define Q-factor? Obtain it for the parallel circuit shown.




- B) A coil of resistance  $20 \Omega$  and inductance  $200 \mu\text{H}$  is in parallel with a variable capacitor. This combination is in series with a resistor of  $8000 \Omega$ . The voltage of the supply is  $200 \text{ V}$  at a frequency of  $106 \text{ Hz}$ . Determine (i) the value of C to give resonance (ii) the Q of the coil (iii) the current in each branch of the circuit at resonance. 7M
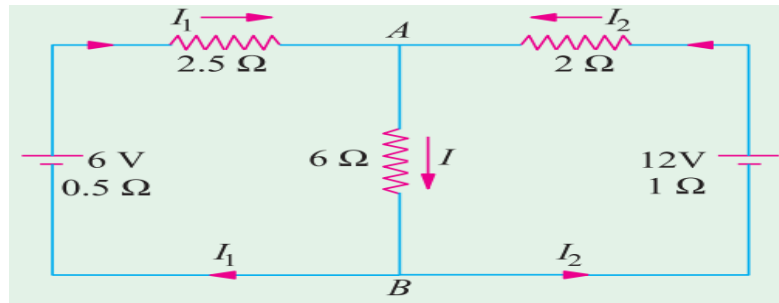
#### UNIT -IV

- 7 A) Illustrate the statement of Superposition theorem and verify it for the circuit shown.



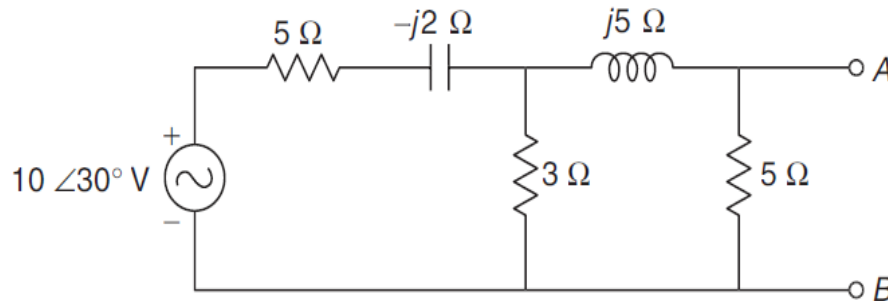
- B) Illustrate Thevenin's Theorem statement and verify it for the circuit shown.



**OR**


- 8 A) Illustrate Norton's Theorem statement and prove it with a suitable circuit for dc excitation. 7M

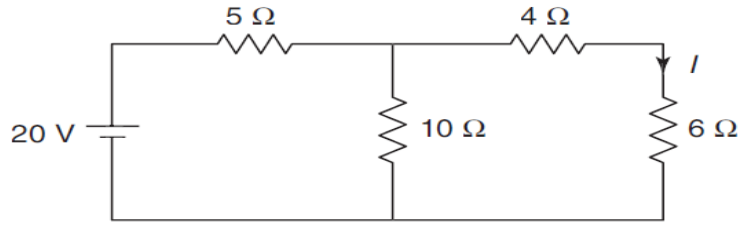- B) Estimate the current I and verify the reciprocity theorem for the network shown in fig. 7M



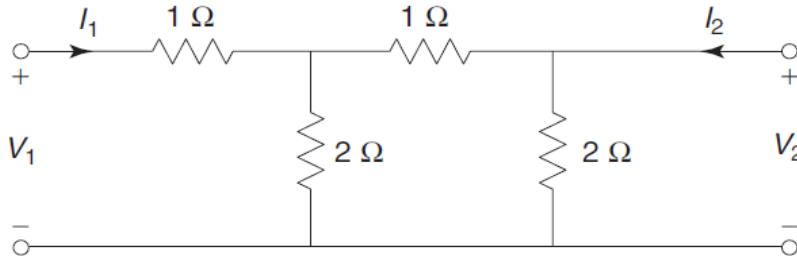
**UNIT -V**

- 9 A) Find Impedance (Z) parameters for the network shown in Fig.



7M

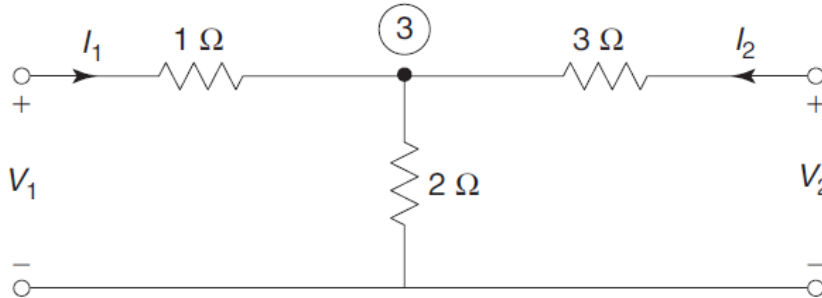- B) Find Admittance (Y) parameters for the network shown in fig.




7M

**OR**

- 10 A) Obtain the necessary condition for reciprocity for Transmission (ABCD) parameters.  
 B) Determine hybrid parameters for the network of fig. Determine whether the network is reciprocal.

7M

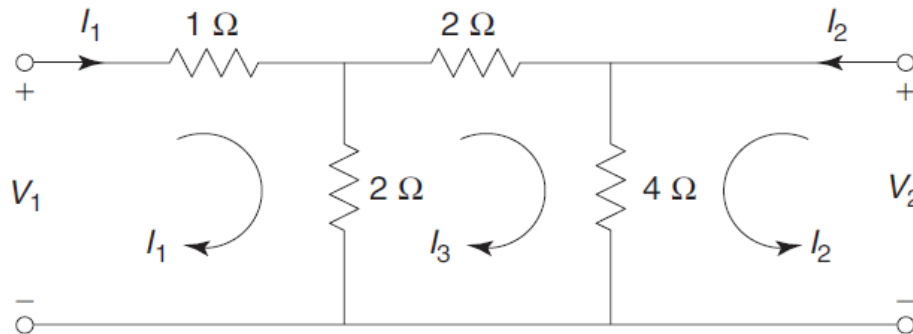

7M